
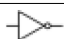



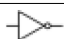



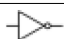





10 Boolean Logic ANSWERS

Question	Answer	Marks										
2	<p>One mark for each correct line</p> <table><thead><tr><th>Logic gate</th><th>Standard symbol</th></tr></thead><tbody><tr><td>AND</td><td></td></tr><tr><td>OR</td><td></td></tr><tr><td>NAND</td><td></td></tr><tr><td>NOT</td><td></td></tr></tbody></table>	Logic gate	Standard symbol	AND		OR		NAND		NOT		4
Logic gate	Standard symbol											
AND												
OR												
NAND												
NOT												

Question	Answer	Marks
7(a)	<p>One mark for each point</p> <ul style="list-style-type: none"> • NOT A • AND B • OR NOT C • expression correct (NOT A AND B) OR NOT C 	4

Question	Answer	Marks																																				
7(b)	<table><tr><th>A</th><th>B</th><th>C</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr></table> <p>4 marks for 8 correct outputs 3 marks for 6/7 correct outputs 2 marks for 4/5 correct outputs 1 mark for 2/3 correct outputs</p>	A	B	C	X	0	0	0	1	0	0	1	0	0	1	0	1	0	1	1	1	1	0	0	1	1	0	1	0	1	1	0	1	1	1	1	0	4
A	B	C	X																																			
0	0	0	1																																			
0	0	1	0																																			
0	1	0	1																																			
0	1	1	1																																			
1	0	0	1																																			
1	0	1	0																																			
1	1	0	1																																			
1	1	1	0																																			

**10 Boolean Logic
ANSWERS**

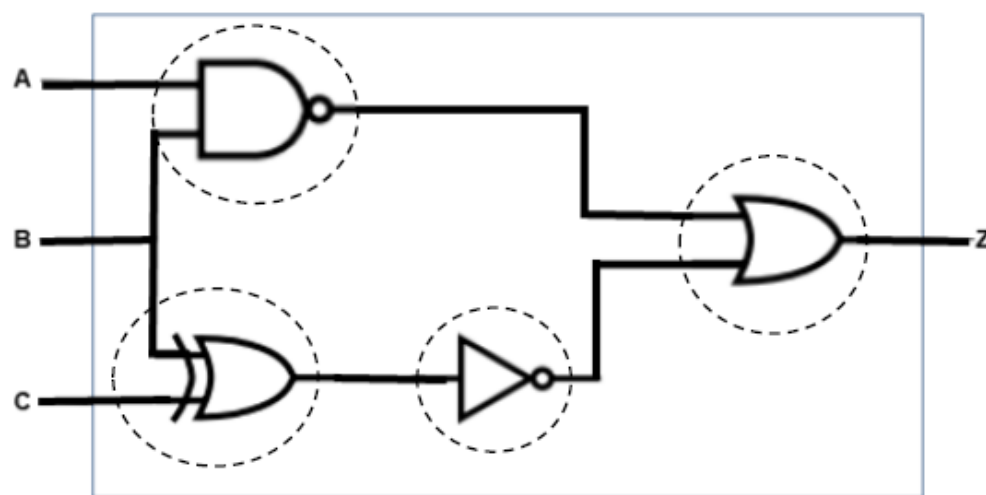Question	Answer	Marks																																				
9(a)	<p>One mark for each correct gate, with the correct input(s) as shown.</p> 	4																																				
9(b)	<p>Four marks for eight correct outputs. Three marks for six or seven correct outputs. Two marks for four or five correct outputs. One mark for two or three correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Z</th></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>1</td></tr></table>	A	B	C	Z	0	0	0	1	0	0	1	1	0	1	0	1	0	1	1	1	1	0	0	1	1	0	1	1	1	1	0	0	1	1	1	1	4
A	B	C	Z																																			
0	0	0	1																																			
0	0	1	1																																			
0	1	0	1																																			
0	1	1	1																																			
1	0	0	1																																			
1	0	1	1																																			
1	1	0	0																																			
1	1	1	1																																			

10 Boolean Logic ANSWERS

Question	Answer	Marks															
6(a)	<p>One mark for correct gate and one mark for correct truth table</p> <p>AND</p> <table border="1"> <thead> <tr> <th>A</th><th>B</th><th>X</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>0</td></tr> <tr> <td>0</td><td>1</td><td>0</td></tr> <tr> <td>1</td><td>0</td><td>0</td></tr> <tr> <td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1	2
A	B	X															
0	0	0															
0	1	0															
1	0	0															
1	1	1															
6(b)	<p>One mark for correct gate and one mark for correct truth table</p> <p>XOR // EOR</p> <table border="1"> <thead> <tr> <th>A</th><th>B</th><th>X</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>0</td></tr> <tr> <td>0</td><td>1</td><td>1</td></tr> <tr> <td>1</td><td>0</td><td>1</td></tr> <tr> <td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	0	2
A	B	X															
0	0	0															
0	1	1															
1	0	1															
1	1	0															

Question	Answer	Marks															
6(c)	<p>One mark for correct gate and one mark for correct truth table</p> <p>NOR</p> <table border="1"> <thead> <tr> <th>A</th><th>B</th><th>X</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>1</td></tr> <tr> <td>0</td><td>1</td><td>0</td></tr> <tr> <td>1</td><td>0</td><td>0</td></tr> <tr> <td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0	2
A	B	X															
0	0	1															
0	1	0															
1	0	0															
1	1	0															
6(d)	<p>One mark for each correct gate, with the correct input(s) as shown.</p>	5															


10 Boolean Logic ANSWERS

Question	Answer	Marks
9(a)	<p>One mark for each correct gate, with the correct input(s) as shown.</p>	4

Question	Answer	Marks																																				
9(b)	<p>Four marks for eight correct outputs. Three marks for six or seven correct outputs. Two marks for four or five correct outputs. One mark for two or three correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Z</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr></table>	A	B	C	Z	0	0	0	0	0	0	1	1	0	1	0	1	0	1	1	0	1	0	0	0	1	0	1	0	1	1	0	1	1	1	1	0	4
A	B	C	Z																																			
0	0	0	0																																			
0	0	1	1																																			
0	1	0	1																																			
0	1	1	0																																			
1	0	0	0																																			
1	0	1	0																																			
1	1	0	1																																			
1	1	1	0																																			

Question	Answer	Marks																																				
8	<p>4 marks for 8 correct outputs 3 marks for 6/7 correct outputs 2 marks for 4/5 correct outputs 1 mark for 2/3 correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr></table>	A	B	C	X	0	0	0	0	0	0	1	0	0	1	0	0	0	1	1	0	1	0	0	0	1	0	1	1	1	1	0	0	1	1	1	0	4
A	B	C	X																																			
0	0	0	0																																			
0	0	1	0																																			
0	1	0	0																																			
0	1	1	0																																			
1	0	0	0																																			
1	0	1	1																																			
1	1	0	0																																			
1	1	1	0																																			

10 Boolean Logic
ANSWERS

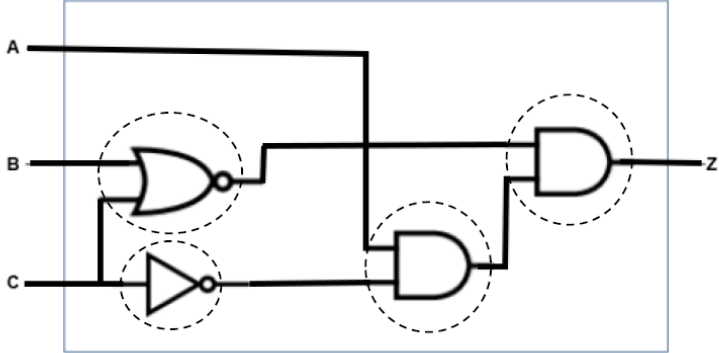Question	Answer	Marks
8(a)	<p>One mark for each correct gate, with the correct input(s) as shown.</p> 	4

Question	Answer	Marks																																				
8(b)	<p>Four marks for eight correct outputs. Three marks for six or seven correct outputs. Two marks for four or five correct outputs. One mark for two or three correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Z</th></tr><tr><td>0</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td></tr></table>	A	B	C	Z	0	0	0	0	0	0	1	0	0	1	0	0	0	1	1	0	1	0	0	1	1	0	1	0	1	1	0	0	1	1	1	0	4
A	B	C	Z																																			
0	0	0	0																																			
0	0	1	0																																			
0	1	0	0																																			
0	1	1	0																																			
1	0	0	1																																			
1	0	1	0																																			
1	1	0	0																																			
1	1	1	0																																			

**10 Boolean Logic
ANSWERS**

Answer				Marks
				3
Truth table			Logic gate	
A	B	Output	NAND	[1]
0	0	1		
0	1	1		
1	0	1		
1	1	0		
A	B	Output	XOR / Exclusive OR	[1]
0	0	0		
0	1	1		
1	0	1		
1	1	0		
A	B	Output	NOR	[1]
0	0	1		
0	1	0		
1	0	0		
1	1	0		

Question	Answer	Marks
5(a)	<p>One mark for each correct logic gate with correct input(s)</p>	6
5(b)	<p>Any one from:</p> <ul style="list-style-type: none"> • NOR • XOR // EOR 	1

10 Boolean Logic

ANSWERS

Question	Answer	Marks																																													
5(c)	<p>Four marks for 8 correct outputs Three marks for 6/7 correct outputs Two marks for 4/5 correct outputs One mark for 2/3 correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table>	A	B	C	Working space	X	0	0	0		1	0	0	1		1	0	1	0		1	0	1	1		1	1	0	0		1	1	0	1		1	1	1	0		0	1	1	1		1	4
A	B	C	Working space	X																																											
0	0	0		1																																											
0	0	1		1																																											
0	1	0		1																																											
0	1	1		1																																											
1	0	0		1																																											
1	0	1		1																																											
1	1	0		0																																											
1	1	1		1																																											

Question	Answer	Marks																				
7(a)	<p>One mark for each correct row</p> <table><thead><tr><th>Statement</th><th>NAND (✓)</th><th>OR (✓)</th><th>XOR (✓)</th></tr></thead><tbody><tr><td>if both inputs are 1, the output is 1</td><td></td><td>✓</td><td></td></tr><tr><td>if both inputs are different from each other, the output is 1</td><td>✓</td><td>✓</td><td>✓</td></tr><tr><td>if both inputs are 0, the output is 0</td><td></td><td>✓</td><td>✓</td></tr><tr><td>if both inputs are the same as each other, the output is always 0</td><td></td><td></td><td>✓</td></tr></tbody></table>	Statement	NAND (✓)	OR (✓)	XOR (✓)	if both inputs are 1, the output is 1		✓		if both inputs are different from each other, the output is 1	✓	✓	✓	if both inputs are 0, the output is 0		✓	✓	if both inputs are the same as each other, the output is always 0			✓	4
Statement	NAND (✓)	OR (✓)	XOR (✓)																			
if both inputs are 1, the output is 1		✓																				
if both inputs are different from each other, the output is 1	✓	✓	✓																			
if both inputs are 0, the output is 0		✓	✓																			
if both inputs are the same as each other, the output is always 0			✓																			
7(b)	<p>One mark for a correct logic gate, one mark for a corresponding truth table</p> <ul style="list-style-type: none">AND <table><thead><tr><th>A</th><th>B</th><th>Output</th></tr></thead><tbody><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></tbody></table>	A	B	Output	0	0	0	0	1	0	1	0	0	1	1	1	2					
A	B	Output																				
0	0	0																				
0	1	0																				
1	0	0																				
1	1	1																				

Question	Answer	Marks
5(a)	<p>One mark for each correct logic gate with the correct inputs</p>	6

10 Boolean Logic ANSWERS

Question	Answer	Marks																																													
5(b)	<p>Four marks for 8 correct outputs Three marks for 6/7 correct outputs Two marks for 4/5 correct outputs One mark for 2/3 correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td></tr></table>	A	B	C	Working space	X	0	0	0		1	0	0	1		0	0	1	0		1	0	1	1		1	1	0	0		0	1	0	1		1	1	1	0		0	1	1	1		0	4
A	B	C	Working space	X																																											
0	0	0		1																																											
0	0	1		0																																											
0	1	0		1																																											
0	1	1		1																																											
1	0	0		0																																											
1	0	1		1																																											
1	1	0		0																																											
1	1	1		0																																											

Question	Answer	Marks
8(a)	<p>One mark for each correct logic gate with correct input(s)</p>	6

Question	Answer	Marks																																													
8(b)	<p>Four marks for 8 correct outputs Three marks for 6/7 correct outputs Two marks for 4/5 correct outputs One mark for 2/3 correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table>	A	B	C	Working space	X	0	0	0		0	0	0	1		1	0	1	0		0	0	1	1		1	1	0	0		0	1	0	1		1	1	1	0		0	1	1	1		1	4
A	B	C	Working space	X																																											
0	0	0		0																																											
0	0	1		1																																											
0	1	0		0																																											
0	1	1		1																																											
1	0	0		0																																											
1	0	1		1																																											
1	1	0		0																																											
1	1	1		1																																											

10 Boolean Logic ANSWERS

Question	Answer	Marks
5(a)	<p>One mark for each correct logic gate with correct input(s)</p>	5

5(b)

Four marks for 8 correct outputs
Three marks for 6/7 correct outputs
Two marks for 4/5 correct outputs
One mark for 2/3 correct outputs




A	B	C	Working space	X
0	0	0		0
0	0	1		0
0	1	0		0
0	1	1		1
1	0	0		0
1	0	1		0
1	1	0		0
1	1	1		1

4

Question	Answer						Marks	
3(a)	1 mark per row							3
		Inputs	AND	OR	NAND	NOR	XOR	
		A = 1 B = 1	✓	✓				
		A = 0 B = 0			✓	✓		
		A = 1 B = 0		✓	✓		✓	

3(b)	<p>1 mark per gate</p> <ul style="list-style-type: none"> • A XOR B • NOT C • (NOT C) OR B • AND 	4
------	--	---

**10 Boolean Logic
ANSWERS**

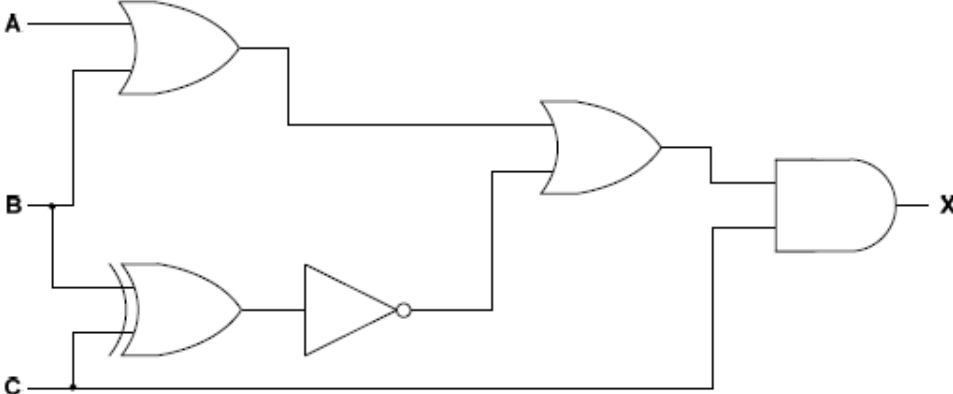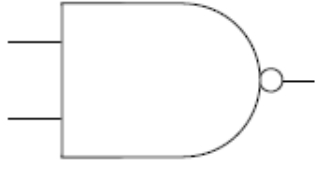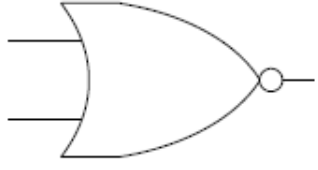Question	Answer	Marks
10(a)	<p>One mark per each correct logic gate with the correct input(s).</p> 	5
10(b)	<p>One mark per logic gate name and one mark per correct drawing.</p> <p>– NAND</p>  <p>– NOR</p> 	2

**10 Boolean Logic
ANSWERS**


Question	Answer					Marks
10(c)	A	B	C	Working space	X	4
	0	0	0		0	
	0	0	1		0	
	0	1	0		0	
	0	1	1		1	
	1	0	0		0	
	1	0	1		1	
	1	1	0		0	
	1	1	1		1	
	4 marks per 8 correct outputs 3 marks per 6/7 correct outputs 2 marks per 4/5 correct outputs 1 mark per 2/3 correct outputs					

Question	Answer	Marks
11(a)	<p>One mark per each correct logic gate with correct input(s)</p>	5



10 Boolean Logic
ANSWERS

Question	Answer	Marks																																													
11(b)	<p>4 marks for 8 correct outputs 3 marks for 6/7 correct outputs 2 marks for 4/5 correct outputs 1 mark for 2/3 correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>0</td></tr></table>	A	B	C	Working space	X	0	0	0		1	0	0	1		1	0	1	0		1	0	1	1		1	1	0	0		1	1	0	1		1	1	1	0		1	1	1	1		0	4
A	B	C	Working space	X																																											
0	0	0		1																																											
0	0	1		1																																											
0	1	0		1																																											
0	1	1		1																																											
1	0	0		1																																											
1	0	1		1																																											
1	1	0		1																																											
1	1	1		0																																											
11(c)	<p>– NOR – XOR / EOR</p>	2																																													

**10 Boolean Logic
ANSWERS**

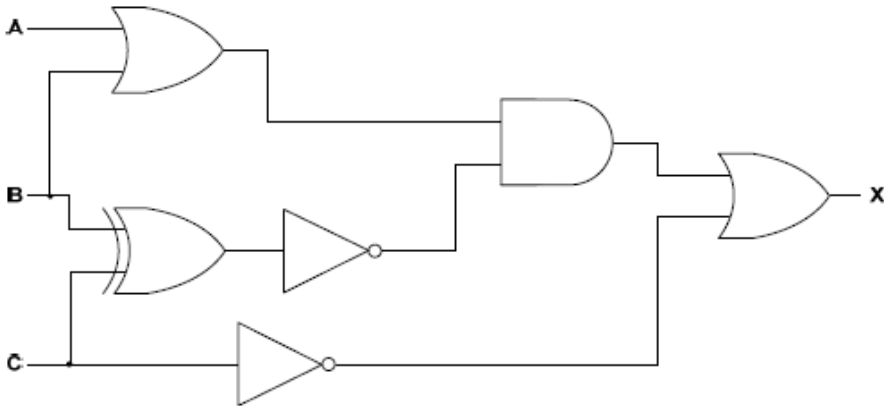
Question	Answer	Marks																																													
8(a)	<p>One mark per each correct logic gate with correct inputs</p> 	6																																													
8(b)	<p>4 marks for 8 correct outputs 3 marks for 6/7 correct outputs 2 marks for 4/5 correct outputs 1 mark for 2/3 correct outputs</p> <table><tr><th>A</th><th>B</th><th>C</th><th>Working space</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td></td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td></td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td><td></td><td>1</td></tr></table>	A	B	C	Working space	X	0	0	0		1	0	0	1		0	0	1	0		1	0	1	1		1	1	0	0		1	1	0	1		0	1	1	0		1	1	1	1		1	4
A	B	C	Working space	X																																											
0	0	0		1																																											
0	0	1		0																																											
0	1	0		1																																											
0	1	1		1																																											
1	0	0		1																																											
1	0	1		0																																											
1	1	0		1																																											
1	1	1		1																																											

**10 Boolean Logic
ANSWERS**

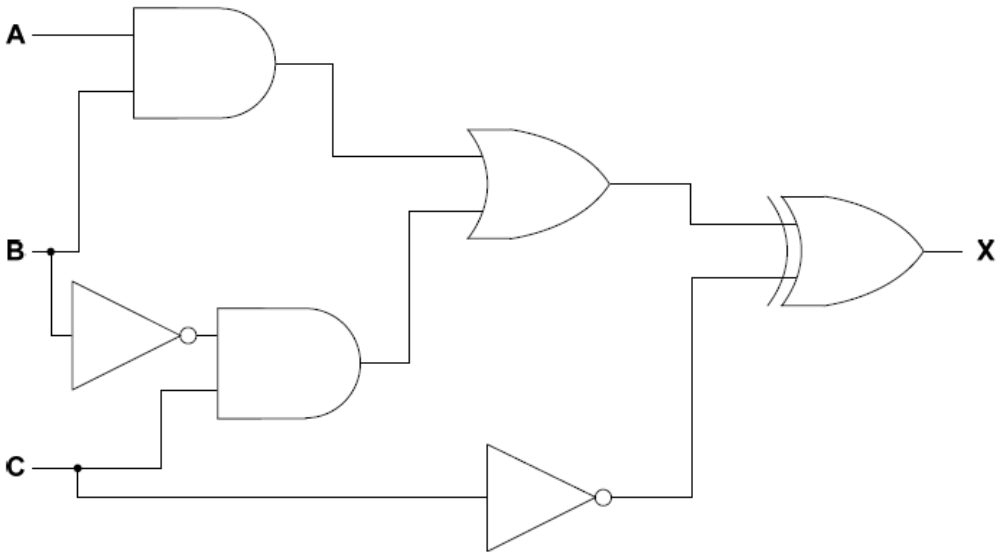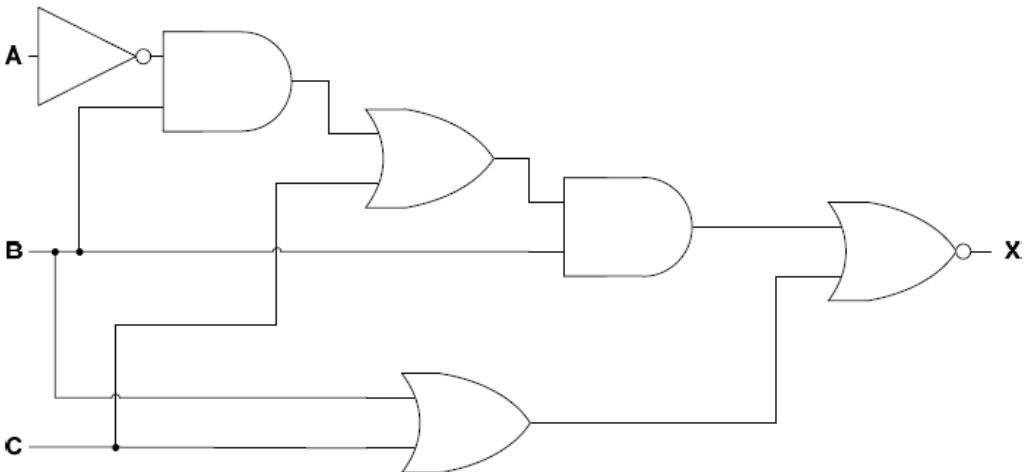Question	Answer	Marks
6(a)	<p>One mark per each correct logic gate, with correct input:</p> 	6
6(b)	<ul style="list-style-type: none"> – Row 1 – Row 3 – Row 4 – Row 5 	4
3(a)	<p>One mark for each correct logic gate with correct input.</p> 	6
3(b)	<p>One mark per each correct row.</p> <ul style="list-style-type: none"> – Row 2 – Row 3 – Row 7 – Row 8 	4

**10 Boolean Logic
ANSWERS**

Question	Answer	Marks
8(a)	<ul style="list-style-type: none"> – AND – NOR – XOR 	3
8(b)	<ul style="list-style-type: none"> – Row 1 – Row 4 – Row 7 – Row 8 	4

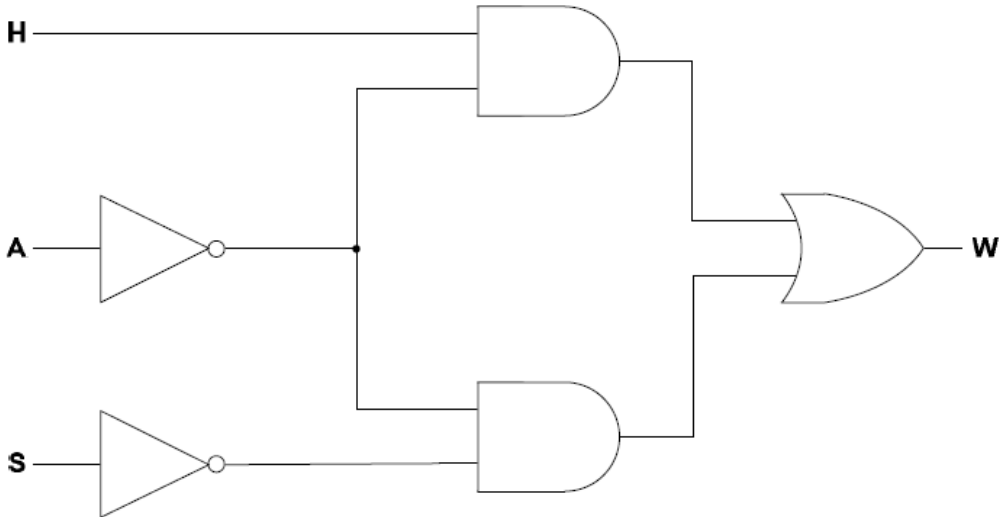Question	Answer	Marks
5(b)	<p>One mark for each logic gates with correct inputs</p>  <pre> graph LR H --- AND1[AND] A --- NOT1[NOT] NOT1 --- AND1 S --- NOT2[NOT] NOT2 --- AND2[AND] AND1 --- OR[OR] AND2 --- OR OR --- W </pre> <ul style="list-style-type: none"> – NOT A – NOT S – H AND NOT A – NOT A AND NOT S – Final OR 	5